

Digital Electronics 2

Lab 2


Sequence of Operations

1. User enters their code for validation
2. User presses the validation push button. If the code is not validated, the user cannot proceed. If it is validated, they can proceed.
3. User can press S (start) to start the circuit. They can then also turn it off with R. While the circuit is running, no modification to the entered code or validation logic will disrupt it. The only way to turn it off is with R (reset).
4. At this point, if the circuit is running, the motor will receive a small amount of voltage that is going through three series resistors.
5. The user can activate the G push button to activate relay 1 and skip the first series resistor. The motor now receives ~4V of power.
6. The user can now activate the H push button to then bypass the second series resistor. The motor now receives ~4 more volts of power.
7. The last relay can be activated with the J pushbutton to activate the last relay and bypass the last series resistor, thus delivering the rest of the voltage to the motor to have it running at 12V.


Simulation Results

1) The circuit is not running, so the motor receives a negligible amount of voltage. 2) The circuit is running, but due to the three series resistors the motor still receives small voltage. 3) The first relay is activated and the first series resistor is bypassed, increasing the voltage by ~4V. 4) The second relay is activated, skipping the second resistor and again increasing voltage to the motor by ~4V. 5) The final relay is activated and the final resistor is skipped, so the motor now receives the full 12V.


1

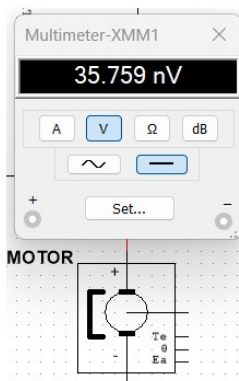


2

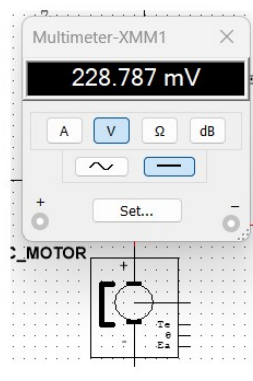


3

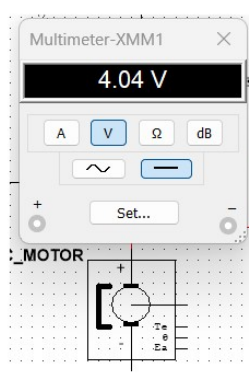

4

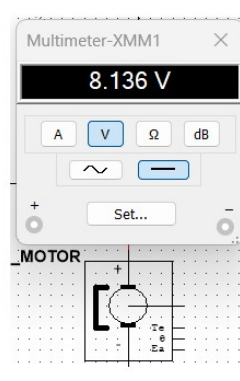

5

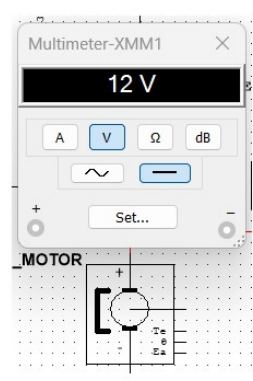

LATCH (Start/Stop) Truth Table

| ENABLE | START | RESET | RUN(next) |
|--------|-------|-------|-----------|
| 0 | 0 | 0 | Hold |
| 0 | 0 | 1 | Reset |
| 0 | 1 | 0 | Hold |
| 0 | 1 | 1 | Reset |
| 1 | 0 | 0 | Hold |
| 1 | 0 | 1 | Reset |
| 1 | 1 | 0 | Set |
| 1 | 1 | 1 | Invalid |

