

Lab 2 Manual

EECE1195: Digital Electronics II

Objectives

This lab extends your knowledge from Lab 1 – Digital Combination Lock by integrating its output with a DC motor soft-starter circuit.

You will design and simulate a combinational logic system with a latching sequential system to control a three-stage DC motor soft start, driven by relay control.

System Description

1. Integration with Lab 1

- The Unlock LED output from your Lab 1 Combination Lock is used as the Enable input for this soft-starter.
 - When the correct 3-digit code is entered and the Test button is pressed, the Unlock LED goes HIGH.
 - That HIGH signal enables the Start/Stop latch in this Lab 2 circuit.
 - Once the motor is running, changes in the code do not affect operation until the Stop button is pressed.
 - After the motor is stopped, the system again checks the Lab 1 Enable signal before any new Start can occur.
 - This ensures security: the motor can only start when the correct code is entered, but accidental code changes during operation will not interrupt running equipment.
-

2. Functional Blocks

A. Start/Stop Control –Latch

- Two momentary pushbuttons: Start (Set) and Stop (Reset).
- The latch output (RUN signal) remains HIGH after Start is pressed and LOW after Stop.
- RUN LED indicates motor ON state.
- RUN output feeds the relay-driver logic that close the motor circuit and start running the motor.
- The latch operates only if the Enable (from Lab 1) = HIGH.

B. Soft-Start Sequence – Three Resistor Stages

- The motor is powered through three series resistors (R_1 , R_2 , R_3) at startup.
- Relay 1, Relay 2, Relay 3 each have a normally open (NO) contact across one resistor.
- When the system starts, relays energize one by one, gradually bypassing the resistors to increase voltage and speed:
 1. Stage 1: All three resistors in series → minimum current (motor begins turning).
 2. Stage 2: Relay 1 ON → R_1 bypassed.
 3. Stage 3: Relay 2 ON → R_2 bypassed.
 4. Stage 4: Relay 3 ON → R_3 bypassed → motor at full voltage.
- Voltage across the motor and the current through the motor must be measured using Digital Multimeters.

C. Relay Driver –Transistor / Transistor Array

- Each relay coil is driven by a transistor or one channel of a ULN2003 transistor array.
- The transistor input or ULN2003 inputs receive logic signals from your circuit, and its outputs energize the relay coils.
- Fly-back diodes across the relay coils are needed to protect your logic circuit from inductive spikes.

D. Power Components

- Select a 12 V DC motor (obtain its datasheet).
- Determine R_1 , R_2 , R_3 values based on motor rated current.
 - Example: $R = \frac{V_{drop}}{I_{motor}}$
 - Ensure $P = I^2 R \geq$ resistor power rating.
- Choose 12 V relays with coil current < 500 mA.

Process Sequence (System Operation)

- 1. Code Entry (Lab 1):**
 - Student enters their 3-digit code using DIP switches.
 - Press Test → If code matches → Unlock LED = HIGH (Enable = 1).
- 2. Ready State:**
 - Enable = 1 and system awaiting Start.
 - RUN LED OFF.
- 3. Start Sequence:**
 - Press Start → latch sets → RUN LED ON → Run Relay closes the motor circuit.
 - Relays activate sequentially: $R_1 \rightarrow$ bypassed, then $R_2 \rightarrow$ bypassed, then $R_3 \rightarrow$ bypassed.
 - Motor voltage rises gradually to 12 V (soft start achieved).
- 4. Running State:**

- Motor at full speed.
 - If student changes DIP-switch code, system continues running (Enable is not re-checked until stop).
- 5. Stop Sequence:**
- Press Stop → latch resets → RUN LED OFF → Run Relay OFF and opens the motor circuit → motor stops.
 - All relays de-energize → resistors re-inserted.
 - Enable is checked again before any next Start.
-

Design Requirements

- 1. Software: Use Multisim.**
 - 2. Inputs:**
 - Start pushbutton
 - Stop pushbutton
 - Enable signal (from Lab 1 Unlock LED)
 - 3. Outputs:**
 - RUN LED (& Run relay control)
 - Three relay controls
 - 4. Power Stage:**
 - Transistors → Relays → Motor + Resistors.
 - 5. Simulation:** Include realistic relay models and 12 V motor.
 - 6. Labels:** All signals must be named clearly in the simulation.
-

Deliverables

Each student (or pair for bonus) must submit a ZIP folder containing:

- 1. Multisim file (.ms14) – fully labeled circuit.**
- 2. Demonstration Video (1–3 minutes) (MUST with verbal description)**
 - Show Lab 1 Enable going HIGH.
 - Demonstrate Start/Stop operation.
 - Display relays energizing sequentially (soft start).
- 3. Design Report (PDF):**
 - Circuit description and sequence of operation.
 - Latch truth table.
 - Logic expressions for relay control.
 - Power and resistance calculations.
 - Screenshots of simulation results.

4. Component List and Cost Analysis (Table):

- List all components (motor, relays, transistors, resistors, LEDs, ICs, pushbuttons, etc.)
- Include unit cost and total project cost (Digikey online prices).

5. Optional Relay LED Indicators (for visual confirmation).

Bonus (+25%) – Hardware Implementation

Students may work in pairs for hardware construction.

Requirements:

1. Assemble the circuit on breadboard or PCB.
2. Demonstrate Start → soft start → Stop sequence.
3. Use actual ULN2003 chip to drive relays.
4. Record a 2 minute video showing the real operation.
5. Hardware report must include a photo of the assembled circuit and measurements (voltages or currents).

Submission Details

- Due Date: Thursday, February 11, 2026 @ 11:59 PM
- Submission: file via eConestoga including simulation, video, report
- Group Work: Allowed only for hardware implementation (max 2 students)

Extra Notes Paper

[illegible]