Case 2

Each DIP switch matches its correct BCD code, therefore MATCH_CODE produces logic HIGH and LED1 lights up. However, the push button (PB) remains open and as such, LED2 still does not light up and the 7segment display still indicates a locked state

(Correct code = 847 or 1000 0100 0111 in BCD)